



Department of Electrical & Computer Engineering
ENCS4370 - Computer Architecture

Multi Cycle Processor Implementation

Prepared By:

Amr Halahla 1200902

Manar Shawahni 1201086

Instructor: Dr. Ayman Hroub

Date: July 12, 2023

Table of Contents

List Of Figures.....	5
List Of Tables	6
Abstract	7
Introduction	7
Objective.....	7
Introduction to RISC Machines.....	7
Multi Cycle Processors.....	7
Design Specifications and Implementation	9
Processor Properties.....	9
Instruction Types and Formats.....	9
Instruction Set.....	11
Finite State Machine.....	12
Data Path Design and details and description	13
Control Signals needed.....	13
Data Path Design	14
Control Unit Block	14
Components.....	15
Instruction Memory & Data Memory.....	15
Code of instruction memory and data memory	15
Test for instruction memory module	16
Test for data memory module	16
Register File	16
Register File Code.....	17
Test Register File	17
Arithmetic Logical Unit	18
ALU code.....	18
ALU Test.....	18
Extenders	19
Signed Extender.....	19
Signed Extender 14 to 32-bits Code.....	19

.....	19
Signed Extender Test.....	19
Offset Extender	20
Offset Extender Code	20
Shift Extender	20
Shift Extender Code.....	20
Stack Memory.....	21
Stack Memory Code	21
Stack Memory Test.....	21
Multiplexers.....	22
2x1 Mux	22
4x1 Mux	22
8x1 Mux	23
Instruction Register	23
Instruction Register Field	23
PC Register	23
Control Units – Main, PC, and Stack Memory Control	24
Main Control Unit	24
Main Control Signals	24
Logic Equation for Main Control Signals	26
Main Control Unit Code	27
Main Control Unit Test.....	27
PC Control Unit	28
PC Control Truth Table	28
Logic Equations for PC Source Signal	28
PC Control Code	29
PC Control Test.....	29
Stack Memory Control Unit.....	29
Stack Control Code	30
Stack Control Test.....	30
Testing.....	31

Sample instructions for test:	31
Test Result for first and second instructions:	31
Test Result for Third and Fourth instructions:	33
Result for Fifth instruction:	35
Test Result for Sixth instruction:	36
Team Work.....	37
Conclusion	37

List Of Figures

Figure 1: R-Type Format.....	9
Figure 2: I-Type Format.....	10
Figure 3: J-Type Format.....	10
Figure 4: S-Type Format.....	10
Figure 6: Finite State Machine	12
Figure 7: Data Path Design.....	14
Figure 8: Control Unit.....	14
Figure 9: Instruction Memory Module	15
Figure 10: Data Memory Module.....	15
Figure 11: Data Memory Code.....	15
Figure 12: Instruction Memory Code.....	15
Figure 13: Sample Instructions	16
Figure 14: Instruction Memory Test	16
Figure 15: Data Memory Test	16
Figure 16: Register File Module	16
Figure 17: Register Element.....	16
Figure 18: Register File Code	17
Figure 19: Test Register File.....	17
Figure 20: ALU block	18
Figure 21: ALU Code.....	18
Figure 22: ALU test.....	18
Figure 23: Extender	19
Figure 24: Signed Extender Code.....	19
Figure 25: Signed Extender Test	19
Figure 26: Offset Extender Code.....	20
Figure 27: Shift Extender Code	20
Figure 28: Stack Memory Code.....	21
Figure 29: Stack Memory Test	21
Figure 30: 2x1 Mux Block	22
Figure 31: 4x1 Multiplexer Block	22
Figure 32: Instruction Register Block	23
Figure 33: Instruction Register Fields	23
Figure 34: PC Register Block.....	23
Figure 35: Main Control Unit Block.....	24
Figure 37: ALU Operation Signal	26
Figure 36: ALU_Src Signal.....	26
Figure 38: Main Control Unit Code	27
Figure 39: Main Control Unit Test.....	27

Figure 40: PC Control Block.....	28
Figure 41: PC Source Block Diagram	28
Figure 42: PC Source Signal Block	28
Figure 43: PC Control Code	29
Figure 44: PC Control Test.....	29
Figure 45: Stack Control Code.....	30
Figure 46: Stack Control Test 1	30
Figure 47: Stack Control Test 1	30
Figure 48: Stack Control Test 2	30
Figure 49: Sample Instructions to Test	31
Figure 50: Test Result for first and second instructions	31
Figure 51: Result of Third and Fourth instructions	33
Figure 52: Result of Third and Fourth instructions	33
Figure 53: Result for Fifth instruction	35
Figure 54: Test Result for Sixth instruction.....	36
Figure 55: Test Result for Sixth instruction.....	36

List Of Tables

Table 1: Instruction Set	11
Table 2: Main Control Truth Table	24
Table 3: Main Control Truth Table	25
Table 4: PC Control Truth Table	28

Abstract

This report discusses the design, and implementation of a Multi Cycle Processor according to a given RISC instruction set. The design was done by analyzing each instruction, and notice main components it needs. The implementation was done by building the components, then derive the control signals for them. Testing was done for each instruction, and then by applying complete scenarios to the processor and validate the result.

Introduction

Objective

The objective of this project is to successfully design, model and simulate a MIPS Multi-Cycle Processor using Verilog HDL. The design approach was used where each sub-module of the processor was first designed, coded, and tested. Once all sub-modules were designed and determined to be fully functional, they were instantiated into a structural module to form our processor.

Introduction to RISC Machines

RISC is a type of CPU design in which it is believed that a simplified instruction set will enhance performance of the processor. It uses a small, highly-optimized set of instructions rather than a more complex set as found in other processors. The word “reduced” in the name refers to the amount of work for any single instruction set.

Typical features of RISC architecture include: fixed length, standard format, identical general-purpose registers, simple addressing modes, one cycle execution time, and pipelining.

Aside from quicker performance, RISC processor components are generally cheaper to design and produce as they utilize less transistors. RISC is the newer technology and is widely used in the industry compared to other processor types.

Multi Cycle Processors

A multi-cycle processor is a type of processor architecture that divides the execution of instructions into multiple stages or cycles. Each cycle performs a specific operation, allowing instructions to be executed efficiently and enabling more complex instructions to be processed. Using the Multi-cycle approach, different instruction may take different amounts of time to process unlike in the

Single-cycle approach where instruction processing is as fast as the slowest instruction.

In a multi-cycle processor, each instruction goes through several stages, with each stage completing within a single clock cycle. The stages typically include:

1. **Instruction Fetch (IF):** The processor fetches the instruction from memory using the program counter (PC) and increments the PC to point to the next instruction.
2. **Instruction Decode (ID):** The fetched instruction is decoded to determine the operation to be performed. This stage also involves fetching any necessary operands or data from registers.
3. **Execution (EX):** The actual operation specified by the instruction is performed in this stage. It may involve arithmetic calculations, logical operations, or address computations.
4. **Memory Access (MEM):** If the instruction requires accessing memory, such as loading or storing data, it is performed in this stage. Data is read from or written to memory.
5. **Write Back (WB):** The results of the previous stage are written back to the appropriate register(s). This stage updates the register file with the computed values.

Design Specifications and Implementation

Processor Properties

1. The instruction size is 32 bits.
2. 32 32-bit general-purpose registers: from R0 to R31.
3. A special purpose register for the program counter (PC).
4. It has a stack called control stack which saves the return addresses
5. Stack pointer (SP), another special purpose register to point to the top of the control stack. SP holds the address of the empty element on the top of the stack. For simplicity, you can assume a separate on-chip memory for the stack, and the initial value of SP is zero.
6. Four instruction types (R-type, I-type, J-type, and S-type).
7. The processor's ALU has an output signal called "zero" signal, which is asserted when the result of the last ALU operation is zero.
8. Separate data and instructions memories

Instruction Types and Formats

As mentioned above, this ISA has four instruction formats, namely, R-type, I-type, J-type, and S-type. These four types have the following common fields:

- a) **2-bit instruction type** (00: R-Type, 01: J-Type, 10: I-type, 11: S-type)
- b) **5-bit function**, to determine the specific operation of the instruction
- c) **Stop bit**, which is the least significant bit of each instruction binary format, and it is used to mark the end of a function code block. In other words, if the value of this stop bit is "1", this means that this instruction is the last instruction of the function, and hence the execution control should return to the return address which is stored on the top of the control stack.

1. R-Type (Register Type) Formats

- **5-bit Rs1**: first source register
- **5-bit Rd**: destination register
- **5-bit Rs2**: second source register
- 9-bit unused

Function ⁵	Rs1 ⁵	Rd ⁵	Rs2 ⁵	Unused ⁹	Type ²	Stop ¹
-----------------------	------------------	-----------------	------------------	---------------------	-------------------	-------------------

Figure 1: R-Type Format

2. I-Type (Immediate Type) Format

- **5-bit Rs1**: first source register
- **5-bit Rd**: destination register
- **14-bit immediate**: unsigned for logic instructions, and signed otherwise

 


Figure 2: I-Type Format

3. J-Type (Jump Type) Format

- 24-bit signed immediate: jump offset

 


Figure 3: J-Type Format

4. S-Type (Shift Type) Format

- **5-bit Rs1**: first source register
- **5-bit Rd**: destination register
- **5-bit Rs2**: second source register. This register stores the shift amount in case the shift amount is variable and it is calculated at runtime
- **5-bit SA**: the constant shift amount.
- 4-bit unused

 


Figure 4: S-Type Format

Instruction Set

- Table 1 shows the instructions supported by this instruction set, with their meaning and decoding.

No.	Instr	Meaning	Function Value
R-Type Instructions			
1	AND	$\text{Reg(Rd)} = \text{Reg(Rs1)} \& \text{Reg(Rs2)}$	00000
2	ADD	$\text{Reg(Rd)} = \text{Reg(Rs1)} + \text{Reg(Rs2)}$	00001
3	SUB	$\text{Reg(Rd)} = \text{Reg(Rs1)} - \text{Reg(Rs2)}$	00010
4	CMP	zero-signal = $\text{Reg(Rs)} < \text{Reg(Rs2)}$	00011
I-Type Instructions			
5	ANDI	$\text{Reg(Rd)} = \text{Reg(Rs1)} \& \text{Immediate}^{14}$	00000
6	ADDI	$\text{Reg(Rd)} = \text{Reg(Rs1)} + \text{Immediate}^{14}$	00001
7	LW	$\text{Reg(Rd)} = \text{Mem}(\text{Reg(Rs1)} + \text{Imm}^{14})$	00010
8	SW	$\text{Mem}(\text{Reg(Rs1)} + \text{Imm}^{14}) = \text{Reg(Rd)}$	00011
9	BEQ	Branch if $(\text{Reg(Rs1)} == \text{Reg(Rd)})$	00100
J-Type Instructions			
10	J	$\text{PC} = \text{PC} + \text{Immediate}^{24}$	00000
11	JAL	$\text{PC} = \text{PC} + \text{Immediate}^{24}$ Stack.Push (PC + 4)	00001
S-Type Instructions			
12	SLL	$\text{Reg(Rd)} = \text{Reg(Rs1)} \ll \text{SA}^5$	00000
13	SLR	$\text{Reg(Rd)} = \text{Reg(Rs1)} \gg \text{SA}^5$	00001
14	SLLV	$\text{Reg(Rd)} = \text{Reg(Rs1)} \ll \text{Reg(Rs2)}$	00010
15	SLRV	$\text{Reg(Rd)} = \text{Reg(Rs1)} \gg \text{Reg(Rs2)}$	00011

Table 1: Instruction Set

Finite State Machine

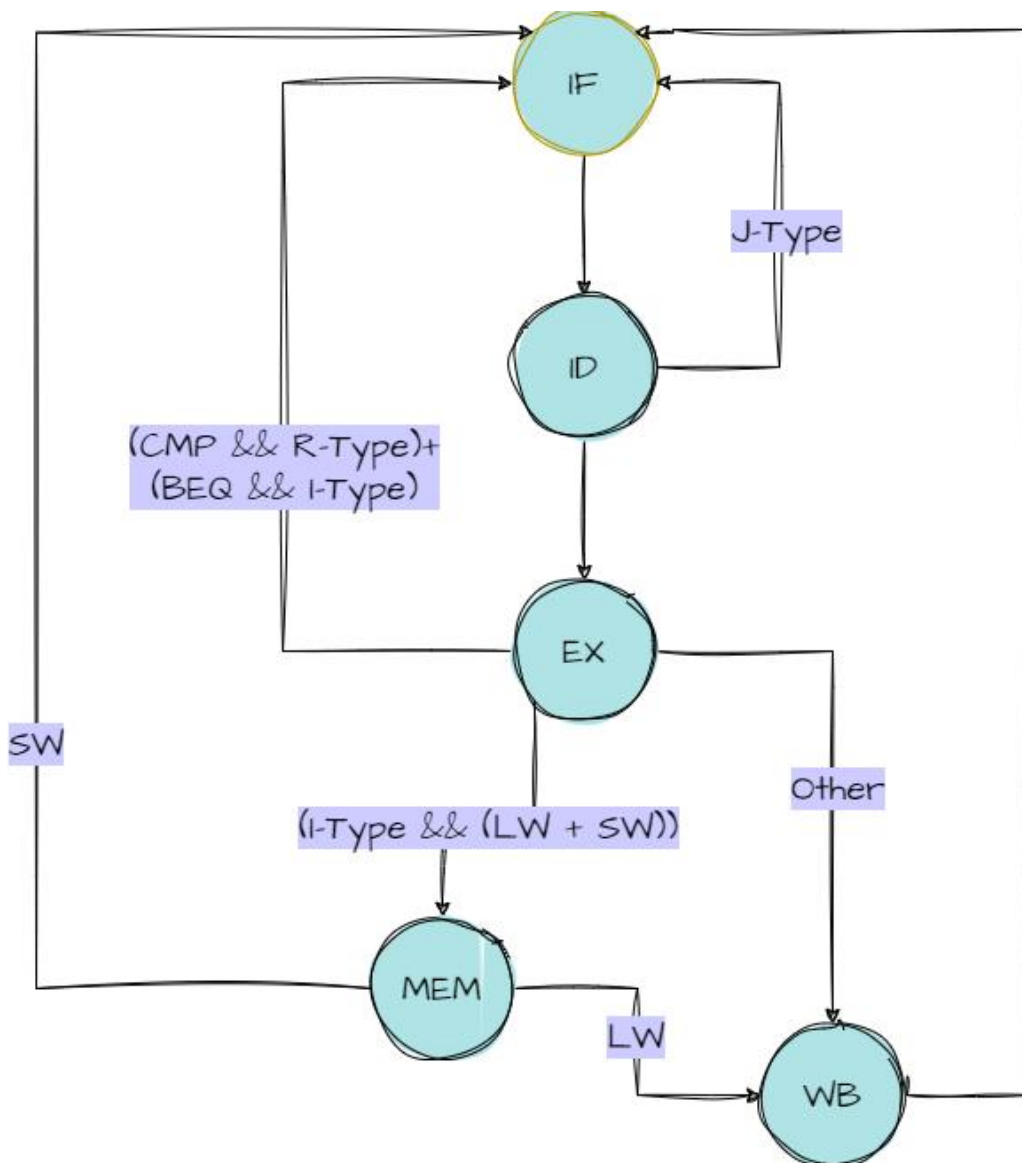


Figure 5: Finite State Machine

Data Path Design and details and description

Control Signals needed

- 1- PC_Src: since there is multiple possible values for the next pc value, a signal is needed to choose the value. The possible options are PC+1, BTA, JA, RA.
 - PC+1: because that the memory cell in our implementation is 32-bits wide, so each instruction is stored in 1 memory cell, so after fetch it, the pc value must be incremented by 1.
 - BTA: it will be used as a next pc value for BEQ instruction if the branch is taken.
 - JA: it will be the next pc value in J-Type instructions.
 - RA: will be used as next pc value if stop bit is 1.
- 2- Reg_Src: Since that CMP instruction is using the Rd as second register operand, then a signal is needed to choose between Rd and Rs2 as a second register to be read from the register file.
- 3- Reg_Write: to prevent and manage the write on register operation, since there are instructions that prevented from write to the register. In opposite, there is other instructions that will write on the register file.
- 4- ALU_Src: The ALU has two inputs, first input is BusA, and the second input has different possible values, so ALU_Src signal will be used to choose the second ALU input between these options: extended-immediate, BusB and Extended-Shift Amount.
- 5- ALU_Op: it will be used to manage the ALU and choose the specific operation to be performed.
- 6- Mem_Read: only LW instruction can read from memory, so this signal will manage the read operation and to prevents the other instructions from read from memory.
- 7- Mem_Write: only SW instruction can Write to memory, so this signal will manage the write operation and to prevents the other instructions from Write to memory.
- 8- WB_Src: to choose the suitable data to be written into the register file, two possible values are ALU_Result and Data_out_of_Memory.
- 9- ExtOp: to decide if the extension operation will be zero or sign extension.

Data Path Design

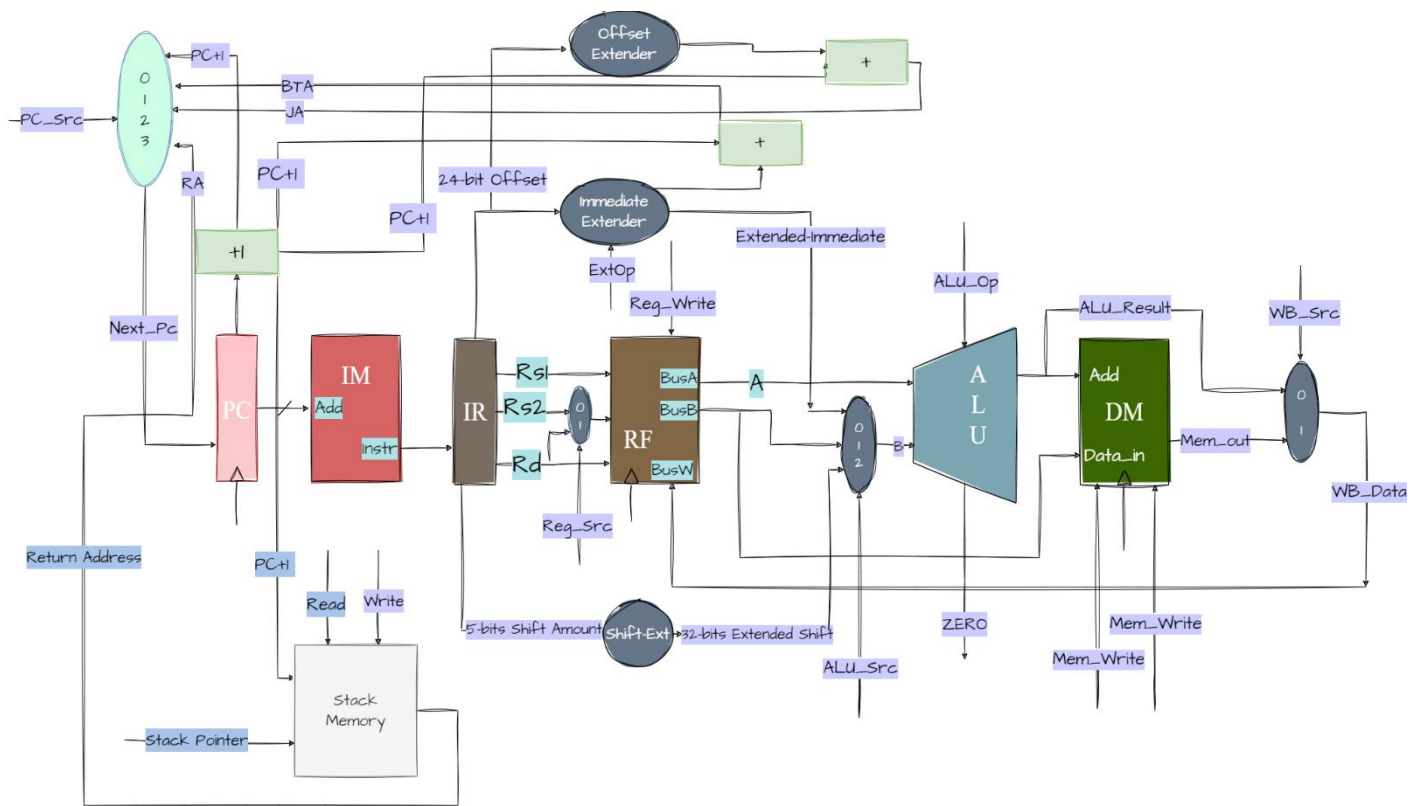


Figure 6: Data Path Design

Control Unit Block

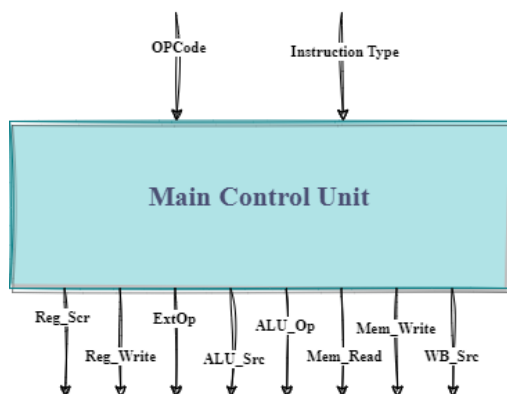


Figure 7: Control Unit

Components

After analyzing the instruction set, we found that the following components are needed.

Instruction Memory & Data Memory

The memories in the implementation are separated into two parts, instruction memory, and data memory. This was done to solve some conflicts, such as, one instruction might be fetching the instruction from the memory and the other instruction is loading/storing some data from/to the memory, so in order to obey the isolation principle, they need to be separated into different memory elements.

 


Figure 8: Instruction Memory Module

 


Figure 9: Data Memory Module

Code of instruction memory and data memory

```
1 module instruction_memory(  
2   input [31:0] addr,  
3   output reg [31:0] data_out  
4 );  
5   reg [31:0] mem [0:1023]; // Assuming 1024 32-bit words in memory  
6  
7   always @(addr) begin  
8     data_out <= mem[addr];  
9   end  
10  
11   initial begin  
12     // Set instructions directly in the memory array  
13     mem[0] = 32'h08CA0052; // addi $5, $3, 10  
14     mem[1] = 32'h0955FFDA; // addi $10, $5, -5  
15     mem[2] = 32'h08061000; // add $3, $2, $1  
16     mem[3] = 32'h00C24000; // and $4, $3, $1  
17     mem[4] = 32'h10C85000; // sub $5, $3, $4  
18     mem[5] = 32'h19060002; // SW $3, 0($4)  
19     mem[6] = 32'h10CC0002; // LW $6, 0($3)  
20   end  
21 endmodule
```

Figure 11: Instruction Memory Code

```
1 module memory (  
2   input clk, input [31:0] addr, input [31:0] data_in,  
3   input write_signal, input read_signal, output reg [31:0] data_out);  
4   // Assuming 1024 32-bit words in memory  
5   reg [31:0] mem [0:1023];  
6   always @(posedge clk) begin  
7     if (write_signal) begin  
8       mem[addr] <= data_in;  
9     end  
10    else if (read_signal) begin  
11      data_out <= mem[addr];  
12    end  
13  end  
14  // Initialize memory with some random values  
15  initial begin  
16    integer i;  
17    for (i = 0; i < 1024; i = i + 1) begin  
18      mem[i] = i;  
19    end  
20  end  
21 endmodule
```

Figure 10: Data Memory Code

Test for instruction memory module

```

initial begin
    // Set instructions directly in the memory
    mem[0] = 32'h08CA0052; // addi $5, $3, 10
    mem[1] = 32'h0955FFDA; // addi $10, $5, -5
    mem[2] = 32'h00861000; // add $3, $2, $1
    mem[3] = 32'h00C24000; // and $4, $3, $1
    mem[4] = 32'h10C85000; // sub $5, $3, $4
    mem[5] = 32'h19060002; // SW $3, 0($4)
    mem[6] = 32'h110C0000; // LW $6, 0($4)
end
    
```

Figure 12: Sample Instructions

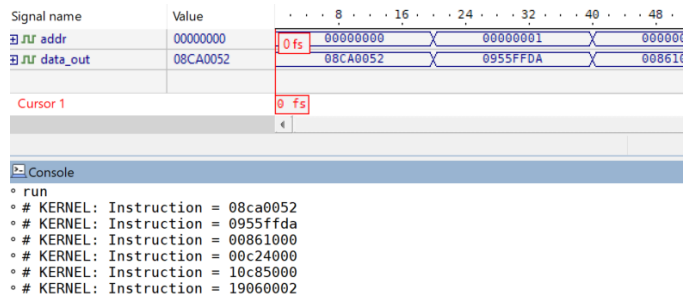


Figure 13: Instruction Memory Test

Test for data memory module

 


Figure 14: Data Memory Test

Register File

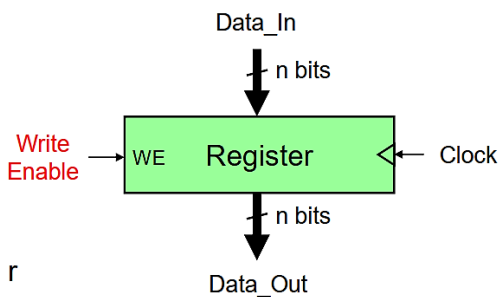


Figure 16: Register Element

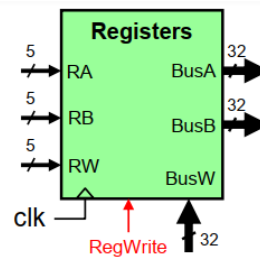


Figure 15: Register File Module

The register file is an essential component in the CPU, providing high-speed storage and quick access to registers for various operations. Its efficient design and close proximity to the execution units contribute to the overall performance and functionality of the computer system.

Register File Code

```

1  module register_file(
2      input clk,
3      input [4:0] read_reg1,
4      input [4:0] read_reg2,
5      input [4:0] write_reg,
6      input [31:0] write_data,
7      input write_enable,
8      output reg [31:0] read_data1,
9      output reg [31:0] read_data2
10 );
11     reg [31:0] registers [0:31];
12
13     always @(posedge clk) begin
14         if (write_enable) begin
15             registers[write_reg] <= write_d
16 ata;
17         end
18         read_data1 = registers[read_reg1];
19         read_data2 = registers[read_reg2];
20     end
21
22     // Initialize register file with some rando
23     m values
24     initial begin
25         registers[0] = 32'h00000000;
26         registers[1] = 32'h00000001;
27         registers[2] = 32'h00000002;
28         registers[3] = 32'h00000003;
29         registers[4] = 32'h00000004;
30         registers[5] = 32'h00000005;
31         registers[6] = 32'h00000006;
32         registers[7] = 32'h00000007;
33         registers[8] = 32'h00000008;
34         registers[9] = 32'h00000009;
35         registers[10] = 32'h0000000A;
36     end
37 endmodule

```

Figure 17: Register File Code

Test Register File

 


Figure 18: Test Register File

Arithmetic Logical Unit

The ALU is a digital circuit within the CPU that executes arithmetic and logical operations on binary data. It takes two input operands, operates on them according to the specified operation, and produces a result. The ALU can perform a wide range of operations, including addition, subtraction, multiplication, division, bitwise logical operations (AND, OR, XOR), and comparisons (such as greater than, less than, equal to).

 


Figure 19: ALU block

ALU code

```

1  module alu(
2      input [31:0] a,
3      input [31:0] b,
4      input [2:0] op,
5      output reg [31:0] out
6  );
7      always @(*) begin
8          case (op)
9              3'b000: out = a + b;
10             3'b001: out = a - b;
11             3'b010: out = a & b;
12             3'b011: out = a << b;
13             3'b100: out = a >> b;
14          endcase
15      end
16  endmodule

```

Figure 20: ALU Code

ALU Test

Signal name	Value	32	64
$\text{JL } a$	00000001	0000000F	00001111 00000001
$\text{JL } b$	00000002	00000004	00000002
$\text{JL } op$	3	0 1 2 3	
$\text{JL } out$	00000004	00000013 0000000B	00000000 00000004

Figure 21: ALU test

Extenders

We used 3 extenders in our data path in order to support all instruction types, for immediate and offset and shift.

 


Figure 22: Extender

Signed Extender

A signed extender is a component or circuit that extends the bit width of a binary number while preserving its interpretation as either a signed or unsigned value.

When extending a binary number, the most significant bit (MSB) is usually replicated to fill the additional bits. This replication is called sign extension or zero extension, depending on whether the original number is interpreted as signed or unsigned.

In our data path, we used the extender to extended the immediate 14-bit to 32-bit, It can be either signed or zero extension, depends on the control signal ExtOp.

Signed Extender 14 to 32-bits Code

```
1 module immediate_extender (  
2     input [13:0] in,  
3     input op,  
4     output reg [31:0] out  
5 );  
6 always @(*) begin  
7     case (op)  
8         // unsigned immediate (zero extend)  
9         2'b0: out = {18'b0, in[13:0]};  
10        // signed immediate (sign extend)  
11        2'b1: out = {{18{in[13]}}, in[13:0]};  
12    endcase  
13 end  
14 endmodule
```

Figure 23: Signed Extender Code

Signed Extender Test

Signal name	Value	8	16	24	32	40	48
in	DEADBEEF	00000000	X	DEADBEEF			
op	1						
out	FFFFFFEF	00000000	X	00003EEF	X	FFFFFFEF	

Figure 24: Signed Extender Test

Offset Extender

used to extend the offset field from 24-bits to 32-bits so that it can be used to calculate the jump address. The input is the offset-24bits field and the output is a 32-bits offset register.

Offset Extender Code




```
1 module offset_extender (
2     input [23:0] in,
3     output reg [31:0] out
4 );
5 always @(*) begin
6     out = {{8{in[23]}}, in[23:0]};
7 end
8 endmodule
```

Figure 25: Offset Extender Code

Shift Extender

We have used a 5 to 32-bits extender to extend the shift amount field so that it can be used as a second ALU operand in shift operations. The input is the Shift Amount 5-bits field, and the output is a shift amount zero extended register.

Shift Extender Code

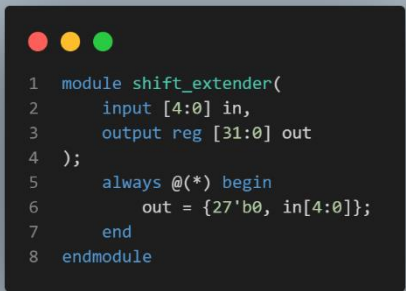

```
1 module shift_extender(
2     input [4:0] in,
3     output reg [31:0] out
4 );
5 always @(*) begin
6     out = {27'b0, in[4:0]};
7 end
8 endmodule
```

Figure 26: Shift Extender Code

Stack Memory

Stack memory, often referred to simply as the stack, is a region of a computer's memory used for dynamic storage allocation and management. It is a fundamental data structure in most programming languages and is crucial for managing function calls, local variables, and supporting nested function execution. We have used the stack memory to store and retrieve the return address and variables with functions, since its efficient for managing function calls and local variables due to its simple and fast LIFO structure. It provides a convenient way to organize and access data within the scope of functions and is an integral part of program execution in most programming languages.

Stack Memory Code

```
1 module stack_memory(  
2     input [31:0] stack_pointer, input pop, input [31:0] data_in,  
3     input push, output reg [31:0] data_out );  
4  
5     reg [31:0] mem [0:1023]; // Assuming 1024 32-bit words in memory  
6     always @(*) begin  
7         if (push) begin  
8             mem[stack_pointer] <= data_in;  
9         end  
10        else if (pop) begin  
11            data_out <= mem[stack_pointer];  
12        end  
13    end  
14    // Initialize memory with some random values  
15    initial begin  
16        integer i;  
17        for (i = 0; i < 1024; i = i + 1) begin  
18            mem[i] = i;  
19        end  
20    end  
21 endmodule
```

Figure 27: Stack Memory Code

Stack Memory Test

Signal name	Value	8	16	24	32	40
stack_pointer	00000000	00000000				
data_in	DEADBEEF	00000000 DEADBEEF				
pop	1					
push	0					
data_out	DEADBEEF	xxxxxxxx DEADBEEF				

Figure 28: Stack Memory Test

Multiplexers

It is a combinational circuit which have many data inputs and single output depending on control or select inputs. For N input lines, $\log n$ (base2) selection lines, or we can say that for 2^n input lines, n selection lines are required.

Multiplexers are also known as **“Data n selector, parallel to serial convertor, many to one circuit, universal logic circuit”**. Multiplexers are mainly used to increase amount of the data that can be sent over the network within certain amount of time and bandwidth.

2x1 Mux

Two 2x1 mux were used in our design of the multicycle processor as shown below:

- 1- Based on the value of the write back source signal, which will be used as the selection line, determine which data will be written into the register file—either the memory output or ALU result.
- 2- Based on the value of the Register Source signal, which will be used as a selection line, determine which register will be read as a second operand from the register file—either Rs2 or Rd.

 


Figure 29: 2x1 Mux Block

4x1 Mux

Two 4x1 mux were used in our design of the multicycle processor as shown below:

- 1- A 4x1 mux has been used to determine the next PC value based on the value of the PC source signal, which has been used as a selection line. The inputs of the mux are [PC+1, BTA, JA, RA], and the next PC will be calculated as a result of the mux operation.
- 2- The other 4x1 Mux has been used to determine the ALU second operand, based on the value the ALU source signal, which has been used as a selection line of the mux. The inputs of the mux are Second Operand Register Rb, Extended immediate, Extended Shift Amount.

 


Figure 30: 4x1 Multiplexer Block

8x1 Mux

One 8x1 Mux has been used in our design of the multi cycle processor, it used to determine the ALU operation to be performed in the ALU, it has 5 inputs are (ADD, AND, SUB, SLL, SLR). the ALU_Op signal has been used as a selection line of 3-bits to determine which operation will be chosen.

Instruction Register

The instruction being executed at the moment is stored in the instruction register (IR), a part of the control unit of a multi-cycle CPU. The decoding of the instruction and selection of the proper control signals for the remainder of the CPU are tasks performed by the IR.

Instruction Register Field

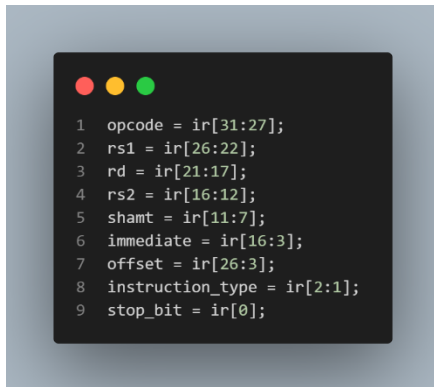


Figure 32: Instruction Register Fields

 


Figure 31: Instruction Register Block

PC Register

The PC (Program Counter) register, also known as the instruction pointer, is a special-purpose register in a CPU (Central Processing Unit). It is used to store the memory address of the next instruction to be fetched and executed by the processor. When the instruction is being executed, the PC register is used to determine the address of the subsequent instruction to be fetched. It allows the processor to sequentially fetch and execute instructions in the correct order, advancing the program execution.

 


Figure 33: PC Register Block

Control Units – Main, PC, and Stack Memory Control

Main Control Unit

Main Control Input

- 5-bit **opcode** field and 2-bit **instruction type** field

Main Control Output

- Main control signals

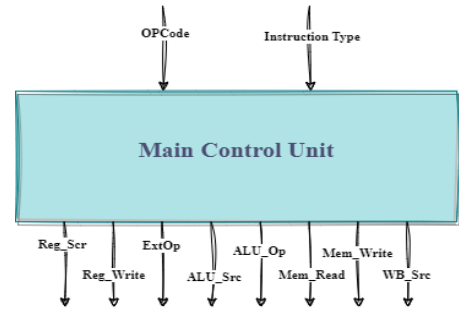


Figure 34: Main Control Unit Block

Main Control Signals

Signal	Effect
Reg_Src	When = 0, Second operand is Rs2 (to be read from RF) When = 1, Second Operand is Rd (to be read from RF)
Reg_Write	When =0, No register is written When = 1, Destination Register Rd is written with the data on BusW
ExtOp	When = 0, 14-bit immediate is Zero-Extended When = 1, 14-bit immediate is Sign-Extended
ALU_Src	When = 00, Second ALU operand is the value of the extended 14-bit immediate When = 01, Second ALU operand is the value of register (Rs2/Rd) that appears on BusB When = 10, Second ALU operand is the value of the extended 5-bit shift amount
Mem_Read	When = 0, Data Memory is NOT read When = 1, Data Memory is read: Mem_out ← Memory [Address]
Mem_Write	When = 0, Data Memory is NOT written When = 1, Data Memory is written: Mem [Address] ← Data_in
WB_Src	When = 0, ALU result will be written on the register: BusW = ALU result When = 1, Data from memory will be written on the register: BusW= Mem_out
ALU_Op	When = 000 => ADD operation will be performed in the ALU When = 001 => SUB operation will be performed in the ALU When = 010 => AND operation will be performed in the ALU When = 011 => Shift Logical Left operation will be performed in the ALU When = 100 => Shift Logical Right operation will be performed in the ALU

Table 2: Main Control Truth Table

Instr_type	Opcode	Reg_Src	Reg_Write	ExtOp	ALU_Src	Mem_Read	Mem_Write	WB_Src	ALU_Op
R	AND	0 = Rs2	1	X	01 = (BusB)	0	0	0 = ALU	010 = AND
R	ADD	0 = Rs2	1	X	01 = (BusB)	0	0	0 = ALU	000 = ADD
R	SUB	0 = Rs2	1	X	01 = (BusB)	0	0	0 = ALU	001 = SUB
R	CMP	0 = Rs2	0	X	01 = (BusB)	0	0	X	001 = SUB
I	ANDI	X	1	0 = Zero	00 = immediate	0	0	0 = ALU	010 = AND
I	ADDI	X	1	1 = Sign	00 = immediate	0	0	0 = ALU	000 = ADD
I	LW	X	1	1 = Sign	00 = immediate	1	0	1 = Mem	000 = ADD
I	SW	X	0	1 = Sign	00 = immediate	0	1	X	000 = ADD
I	BEQ	1 = Rd	0	1 = Sign	01 = BusB	0	0	X	001 = SUB
J	J	X	0	X	X	0	0	X	X
J	JAL	X	0	X	X	0	0	X	X
S	SLL	X	1	X	10 = Shift Amount	0	0	0 = ALU	011 = SLL
S	SLR	X	1	X	10 = Shift Amount	0	0	0 = ALU	100 = SLR
S	SLLV	0 = Rs2	1	X	01 = (BusB)	0	0	0 = ALU	011 = SLL
S	SLRV	0 = Rs2	1	X	01 = (BusB)	0	0	0 = ALU	100 = SLR

Table 3: Main Control Truth Table

Logic Equation for Main Control Signals

- $\text{Reg_Src} = \text{BEQ} \ \&\& \ \text{I-type}$
- $\text{Reg_Write} = (\text{R-Type} \ \&\& \ \sim\text{CMP}) \ || \ (\text{I-type} \ \&\& \ \sim\text{SW}) \ || \ (\text{I-type} \ \&\& \ \sim\text{BEQ}) \ || \ (\text{S-Type})$
- $\text{ExtOp} = \sim (\text{I-Type} \ \&\& \ \text{ANDI})$
- $\text{WB_Src} = \text{SW} \ \&\& \ \text{I-Type}$
- $\text{Mem_Read} = \text{I-Type} \ \&\& \ \text{LW}$
- $\text{Mem_Write} = \text{I-Type} \ \&\& \ \text{SW}$
- $\text{ALU_Src} = \{\text{S1}, \text{S0}\}$

Where:

- $\text{S1} = (\text{S-Type} \ \&\& \ (\text{SLL} \ || \ \text{SLR}))$
- $\text{S0} = (\text{R-Type} \ || \ (\text{I-Type} \ \&\& \ \text{BEQ}) \ || \ (\text{S-Type} \ \&\& \ (\text{SLLV} \ || \ \text{SLRV})))$

- $\text{ALU_Op} = \{\text{S2}, \text{S1}, \text{S0}\}$

Where:

- $\text{S2} = (\text{S-Type} \ \&\& \ (\text{SLR} \ || \ \text{SLRV}))$
- $\text{S1} = (\text{R-Type} \ \&\& \ \text{AND}) \ || \ (\text{I-Type} \ \&\& \ \text{ANDI}) \ || \ (\text{S-Type} \ \&\& \ (\text{SLL} \ || \ \text{SLLV}))$
- $\text{S0} = (\text{R-Type} \ \&\& \ (\text{SUB} \ || \ \text{CMP})) \ || \ (\text{I-Type} \ \&\& \ \text{BEQ}) \ || \ (\text{S-Type} \ \&\& \ (\text{SLL} \ || \ \text{SLLV}))$

 


Figure 35: ALU Operation Signal

 


Figure 36: ALU_Src Signal

Main Control Unit Code

```

1 module control_unit(input [1:0] instr_type, input [4:0] opcode,
2   output reg reg_b,
3   output reg reg_wr,
4   output reg ext_op,
5   output reg [1:0] alu_src,
6   output reg [2:0] alu_op,
7   output reg mem_read,
8   output reg mem_write,
9   output reg wb_src
10 );
11
12 reg s4,s3,s2,s1,s0;
13 always @(*)begin
14   reg_b = (opcode == 5'b00100 && instr_type == 2'b01) ? 1'b1 : 1'b0; // BEQ && I-type
15   reg_wr = (instr_type == 2'b00 && opcode != 5'b00011) || (instr_type == 2'b01 && opcode != 5'b00011 && opcode != 5'b00100) || (instr_type == 2'b11) ? 1'b1 : 1'b0;
16   ext_op = ~(instr_type == 2'b01 && opcode == 5'b00000) ? 1'b1 : 1'b0; // ADDI && I-type
17   s1 = (instr_type == 2'b11 && (opcode == 5'b00000 || opcode == 5'b00001)) ? 1'b1 : 1'b0;
18   s0 = (instr_type == 2'b00 || (instr_type == 2'b01 && opcode == 5'b00100) || (instr_type == 2'b11 && (opcode == 5'b00010 || opcode == 5'b00011))) ? 1'b1 : 1'b0;
19   alu_src = {s1,s0}; // ALU source
20
21   s4 = (instr_type == 2'b11 && (opcode == 5'b00001 || opcode == 5'b00011));
22   s3 = ((instr_type == 2'b00 && opcode == 5'b00000) || (instr_type == 2'b01 && opcode == 5'b00000) || (instr_type == 2'b11 && opcode == 5'b00000) || (instr_type == 2'b11 && opcode == 5'b00010));
23   s2 = ((instr_type == 2'b00 && (opcode == 5'b00010 || opcode == 5'b00011)) || (instr_type == 2'b01 && opcode == 5'b00100) || (instr_type == 2'b11 && opcode == 5'b00000) || (instr_type == 2'b11 && opcode == 5'b00010)) ? 1'b1 : 1'b0;
24   alu_op = {s4,s3,s2}; // ALU operation
25
26   mem_read = (opcode == 5'b00010 && instr_type == 2'b01) ? 1'b1 : 1'b0; // LW && I-type
27   mem_write = (opcode == 5'b00011 && instr_type == 2'b01) ? 1'b1 : 1'b0; // SW && I-type
28   wb_src = (opcode == 5'b00010 && instr_type == 2'b01) ? 1'b1 : 1'b0; // LW && I-type
29 end
30
31 endmodule

```

Figure 37: Main Control Unit Code

Main Control Unit Test

 


Figure 38: Main Control Unit Test

PC Control Unit

PC Control Input

- 5-bit **opcode** field, 2-bit **instruction type** field, 1-bit Zero Signal and Stop bit.

PC Control Output

- PC Source signal

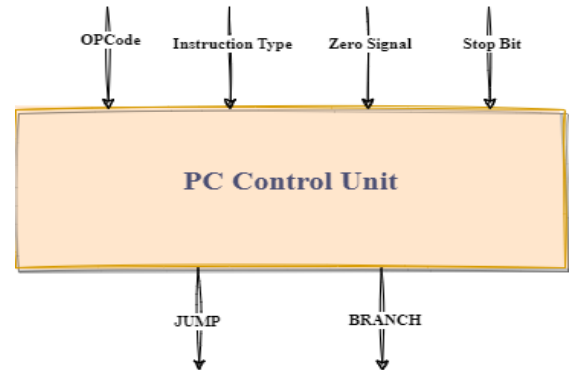


Figure 39: PC Control Block

PC Control Truth Table

OPCode	Type	Zero Signal	Stop bit	JUMP	BRANCH
X	X	X	1	1	1
X	R	X	0	0	0
X	S	X	0	0	0
X	J	X	0	1	0
BEQ	I	0	0	0	0
BEQ	I	1	0	0	1

Table 4: PC Control Truth Table

Logic Equations for PC Source Signal

- $JUMP = J\text{-Type} \mid\mid \text{Stop-bit}$
- $BRANCH = (BEQ \ \&\& \ \text{Zero_Signal} \ \&\& \ I\text{-Type}) \mid\mid \text{Stop-bit}$

 


Figure 41: PC Source Signal Block

 


Figure 40: PC Source Block Diagram

PC Control Code

```
1 module pc_control(input [1:0]instr_type,input [4:0] opcode, input zero_signal, stop_bit, output reg [1:0] pc_src);
2   reg branch;
3   reg jump;
4
5   // MUX to choose the pc_src value
6   always @* begin
7     branch = (instr_type == 2'b01 && zero_signal && opcode == 5'b00100) || stop_bit;
8     jump = (instr_type == 2'b10) || stop_bit;
9     case ({jump, branch})
10      2'b00: pc_src = 2'b00; // pc + 4
11      2'b01: pc_src = 2'b01; // branch taken
12      2'b10: pc_src = 2'b10; // jump
13      2'b11: pc_src = 2'b11; // Return Address
14    endcase
15  end
16 endmodule
```

Figure 42: PC Control Code

PC Control Test

 


Figure 43: PC Control Test

Stack Memory Control Unit

Stack Control Input

- 5-bit **opcode** field, 2-bit **instruction type** field, 1-bit Zero Signal and 32-bits SP.

Stack Control Output

- **Push, Pop** and new value of **SP**.

Stack Control Code

```

1  module stack_control(
2      input [1:0] instr_type,
3      input [4:0] opcode,
4      input stop_bit,
5      input [31:0] sp,
6      output reg push,
7      output reg pop,
8      output reg [31:0] next_sp
9  );
10 always @* begin
11     if (instr_type == 2'b10 && opcode == 5'b00001) begin // JAL
12         push = 1;
13         pop = 0;
14         next_sp = sp + 1; // push return address onto stack
15     end
16     else if(stop_bit) begin // end of function, get return address
17         push = 0;
18         pop = 1;
19         next_sp = sp - 1; // pop return address off stack
20     end
21     else begin
22         push = 0;
23         pop = 0;
24         next_sp = sp;
25     end
26 end
27 endmodule

```

Figure 44: Stack Control Code

Stack Control Test

 


Figure 45: Stack Control Test 1

 


Figure 47: Stack Control Test 2

Testing

Sample instructions for test:

```

1 mem[0] = 32'h08CA0052; // addi $5, $3, 10 => 32'b00001(opcode)00011(rs1)00101(rd)00000000001010(immediate)01(type)0(stop)
2 mem[1] = 32'h0955FFDA; // addi $10, $5, -5 => 32'b00001(opcode)00101(rs1)01010(rd)1111111111011(immediate)01(type)0(stop)
3 mem[2] = 32'h08B1000; // add $3, $2, $1 => 32'b00001(opcode)00010(rs1)00011(rd)00001(rs2)000000000(unused)00(type)0(stop)
4 mem[3] = 32'h0C81000; // and $4, $3, $1 => 32'b00000(opcode)00011(rs1)00100(rd)00001(rs2)000000000(unused)00(type)0(stop)
5 mem[4] = 32'h10CA4000; // sub $5, $3, $4 => 32'b00010(opcode)00011(rs1)00101(rd)00100(rs2)000000000(unused)00(type)0(stop)
6 mem[5] = 32'h19060002; // SW $3, 0($4) => 32'b00011(opcode)00100(rs1)00011(rd)00000000000000(imm)01(type)0(stop)
7 mem[6] = 32'h110C0002; // LW $6, 0($4) => 32'b00010(opcode)00100(rs1)00110(rd)00000000000000(imm)01(type)0(stop)

```

Figure 48: Sample Instructions to Test

Note: Data memory and registers are all initialized with value as same as its address:

Mem[i] = i, Register[i] = i

Test Result for first and second instructions:

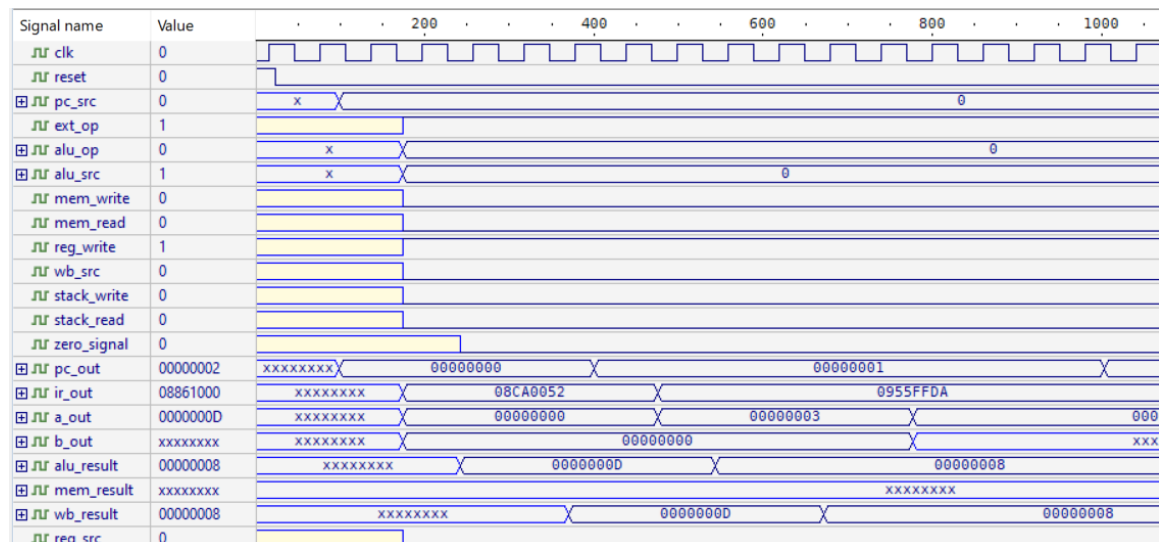


Figure 49: Test Result for first and second instructions

1- After execute first instruction: addi \$5, \$3, 10:

- PC_out = Current PC = 0
- ExtOp = 1 (Add operation => sign extension for immediate field)
- ALU_Op = 0 => Add operation
- ALU_Src = 0 => Extended Immediate
- Mem_Read = Mem_Write = 0 => No memory access
- Reg_Write = 1 => instruction writes on register file
- Reg_Src = 0 => has no effect on this instruction
- WB_Src = 0 => the data to be write on the register is ALU result
- Stack (Read and Write) = 0 => No stack operations
- Zero_signal = 0 => it has no effect in the instruction

Result of the instruction:

- As shown in the wave form, ALU Result = 0xD, as follow:
- $\$S3 = 0x3$
- $\text{Addi } \$S5, \$S3, 10 \Rightarrow \$S5 = 3 + 10 = 13 \Rightarrow 0xD$
- $\text{WB_Data} = 0xD$

2- After execute second instruction: $\text{addi } \$10, \$5, -5$:

- a. $\text{PC_out} = \text{Current PC} = 1$
- b. $\text{ExtOp} = 1$ (Add operation \Rightarrow sign extension for immediate field)
- c. $\text{ALU_Op} = 0 \Rightarrow$ Add operation
- d. $\text{ALU_Src} = 0 \Rightarrow$ Extended Immediate
- e. $\text{Mem_Read} = \text{Mem_Write} = 0 \Rightarrow$ No memory access
- f. $\text{Reg_Write} = 1 \Rightarrow$ instruction writes on register file
- g. $\text{Reg_Src} = 0 \Rightarrow$ has no effect on this instruction
- h. $\text{WB_Src} = 0 \Rightarrow$ the data to be write on the register is ALU result
- i. $\text{Stack (Read and Write)} = 0 \Rightarrow$ No stack operations
- j. $\text{Zero_signal} = 0 \Rightarrow$ it has no effect in the instruction

Result of the instruction:

- As shown in the wave form, ALU Result = 0xD, as follow:
- $\$S5 = 0xD \Rightarrow$ result of previous instruction
- $\text{Addi } \$S10, \$S5, 5 \Rightarrow \$S10 = 13 - 5 = 8 \Rightarrow 0x8$
- $\text{WB_Data} = 0x8$

Test Result for Third and Fourth instructions:

 


Figure 50: Result of Third and Fourth instructions

- After execute Third instruction: add \$3, \$2, \$1:
 - PC_out = Current PC = 2
 - ExtOp = 1 has no effect (didn't changed from previous instruction)
 - ALU_Op = 0 => Add operation
 - ALU_Src = 1 => BusB (register \$S1)
 - Mem_Read = Mem_Write = 0 => No memory access
 - Reg_Write = 1 => instruction writes on register file
 - Reg_Src = 0 => Rs2
 - WB_Src = 0 => the data to be write on the register is ALU result
 - Stack (Read and Write) = 0 => No stack operations
 - Zero_signal = 0 => it has no effect in the instruction

Result of the instruction:

- As shown in the wave form, ALU Result = 0x3, as follow:
- \$S2 = 0x2, \$S1 = 0x1
- Add \$S3, \$S2, \$S1 => \$S3 = 1 + 2 = 3 => 0x3
- WB_Data = 0x3

2- After execute Forth instruction: and \$4, \$3, \$1:

- PC_out = Current PC = 3
- ExtOp = 1 has no effect (didn't changed from previous instruction)
- ALU_Op = 2 => And operation
- ALU_Src = 1 => BusB (register \$S1)
- Mem_Read = Mem_Write = 0 => No memory access
- Reg_Write = 1 => instruction writes on register file
- Reg_Src = 0 => Rs2
- WB_Src = 0 => the data to be write on the register is ALU result
- Stack (Read and Write) = 0 => No stack operations
- Zero_signal = 0 => it has no effect in the instruction

Result of the instruction:

- As shown in the wave form, ALU Result = 0xD, as follow:
- \$S3 = 0x3, \$S1 = 0x1
- And \$S4, \$S3, \$S1 => \$S4 = 0x3 & 0x1 = 1 => 0x1
- WB_Data = 0x1

Result for Fifth instruction:

 


Figure 52: Result for Fifth instruction

After execute Fifth instruction: sub \$5, \$3, \$4:

- PC_out = Current PC = 0x4
- ExtOp = 1 has no effect (didn't changed from previous instruction)
- ALU_Op = 1 => Sub operation
- ALU_Src = 1 => BusB (register \$S1)
- Mem_Read = Mem_Write = 0 => No memory access
- Reg_Write = 1 => instruction writes on register file
- Reg_Src = 0 => Rs2
- WB_Src = 0 => the data to be write on the register is ALU result
- Stack (Read and Write) = 0 => No stack operations
- Zero_signal = 0 => it has no effect in the instruction
- Mem_out = x

Result of the instruction:

- As shown in the wave form, ALU Result = 0x2, as follow:
- \$S3 = 0x3, \$S4 = 0x1
- Sub \$S5, \$S3, \$S4 => \$S5 = 0x3 - 0x1 = 2 => 0x2
- WB_Data = 0x2

Test Result for Sixth instruction:

 


Figure 53: Test Result for Sixth instruction

After execute Sixth instruction: SW \$3, 0(\$4):

- PC_out = Current PC = 0x5
- ExtOp = 1 => Sign extension
- ALU_Op = 0 => Addition (calculate memory address)
- ALU_Src = 0 => extended immediate
- Mem_Read = 0 => prevent read from memory
- Mem_Write = 1 => Write on memory
- Reg_Write = 0 => No write on register file
- Reg_Src = 0 => has no effect (didn't changed)
- WB_Src = 0 => has no effect (didn't changed)
- Stack (Read and Write) = 0 => No stack operations
- Zero_signal = 0 => it has no effect in the instruction
- Mem_out = x

Result of the instruction:

- As shown in the wave form, ALU Result = 0x1, as follow:
- Extended immediate = 0, \$S4 = 1
- Memory address = ALU Result = 0 + \$S4 = 1
- WB_Data = 0x2 (didn't changed) => will not be written

Team Work

We have done all work together; it was all shared between us.

Conclusion

The design for a multi-cycle system must be precise and accurate, and it requires a large number of components.

NOTE: some delays has been added for each execution stage to make a correction of flow of the instruction execution and to prevent glitches, also to give enough time for read and write operations and prevent conflicts.